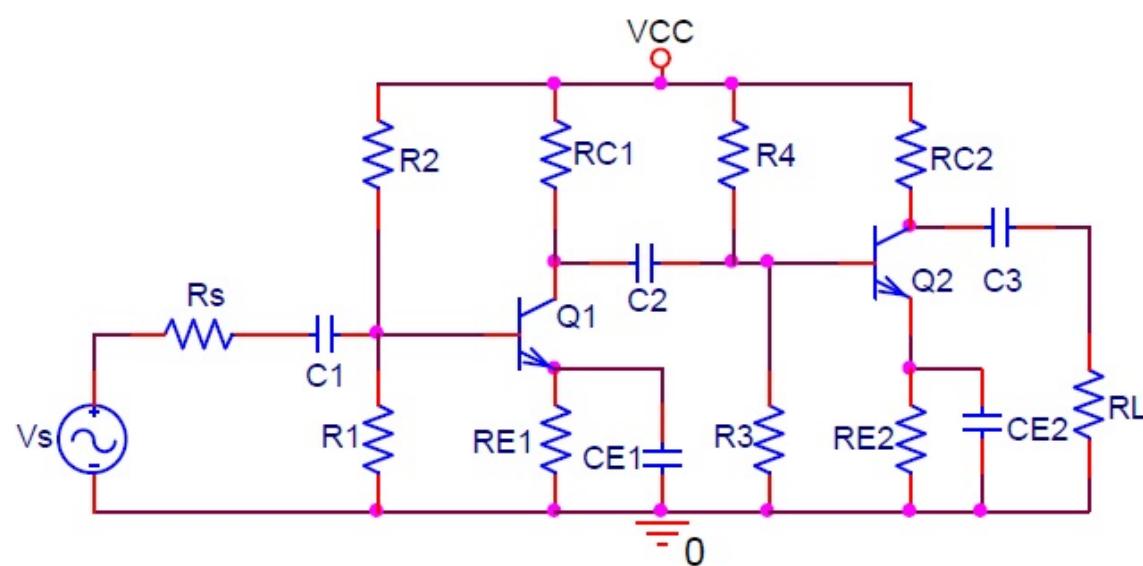


Realizo el análisis del siguiente amplificador:



$$\begin{aligned}R_s &= 50\Omega, \quad V_{CC} = 10V \\R_1 &= 1K\Omega, \quad \beta_1 = \beta_2 = 100 \\R_2 &= 2.3K\Omega, \quad C_1 = 1\mu F \\R_{E1} &= 100\Omega, \quad C_2 = 2\mu F \\R_{C1} &= 200\Omega, \quad C_3 = 10\mu F \\R_3 &= 10K\Omega, \quad C_{E1} = 5\mu F \\R_4 &= 90K\Omega, \quad C_{E2} = 10\mu F \\R_{E2} &= 500\Omega, \quad C_o = \text{despreciable} \\R_{C2} &= 5K\Omega, \quad C_{bc} = 10pF \\R_L &= 5K\Omega, \quad f_T = 500MHz, \quad \omega_T = 2\pi f_T.\end{aligned}$$

Análisis de frecuencias medias

Análisis D.C

Ejemplo 1

$$R_{B1} = R_1 \parallel R_2 \approx 696\Omega$$

$$V_{BB1} = \frac{V_{CC}R_1}{R_1 + R_2} = 3.03(V)$$

Ejemplo 2

$$R_{B2} = R_3 \parallel R_4 = 9K\Omega$$

$$V_{BB2} = \frac{V_{CC}R_3}{R_3 + R_4} = 1(V)$$

L.V.K en 1º malla de entrada:

$$V_{BB_1} = \frac{I_{CQ_1} R_{B_1}}{\beta} + V_{BE} + I_{CQ_1} R_{E_1}$$

$$\Rightarrow I_{CQ_1} = \frac{V_{BB_1} - V_{BE}}{\frac{R_{B_1}}{\beta} + R_{E_1}} = 21.7 \text{ mA}$$

L.V.K en 1º malla de salida:

$$V_{CC} = I_C R_{C_1} + V_{CE_1} + I_C R_{E_1}$$

$$\Rightarrow V_{CEQ_1} = V_{CC} - I_{CQ_1} (R_{C_1} + R_{E_1})$$

$$\Rightarrow V_{CEQ_1} = 3.49 \text{ (V)}$$

$$V_{CEmax_1} = V_{CC} = 10 \text{ (V)}$$

$$I_{Cmax_1} = \frac{V_{CC}}{R_{C_1} + R_{E_1}} = 33.3 \text{ mA}$$

L.V.K en 1º malla de salida:

$$\Rightarrow I_{CQ_2} = \frac{V_{BB_2} - V_{BE}}{\frac{R_{B_2}}{\beta} + R_{E_2}} = 508.5 \text{ mA}$$

L.V.K en malla de salida:



$$\Rightarrow V_{CEQ_2} = V_{CC} - I_{CQ_2} (R_{C_2} + R_{E_2})$$

$$\Rightarrow V_{CEQ_2} = 7.2 \text{ (V)}$$

$$V_{CEmax_2} = V_{CC} = 10 \text{ (V)}$$


$$I_{Cmax_2} = \frac{V_{CC}}{R_{C_2} + R_{E_2}} = 1.8 \text{ mA}$$

La Recta DC :

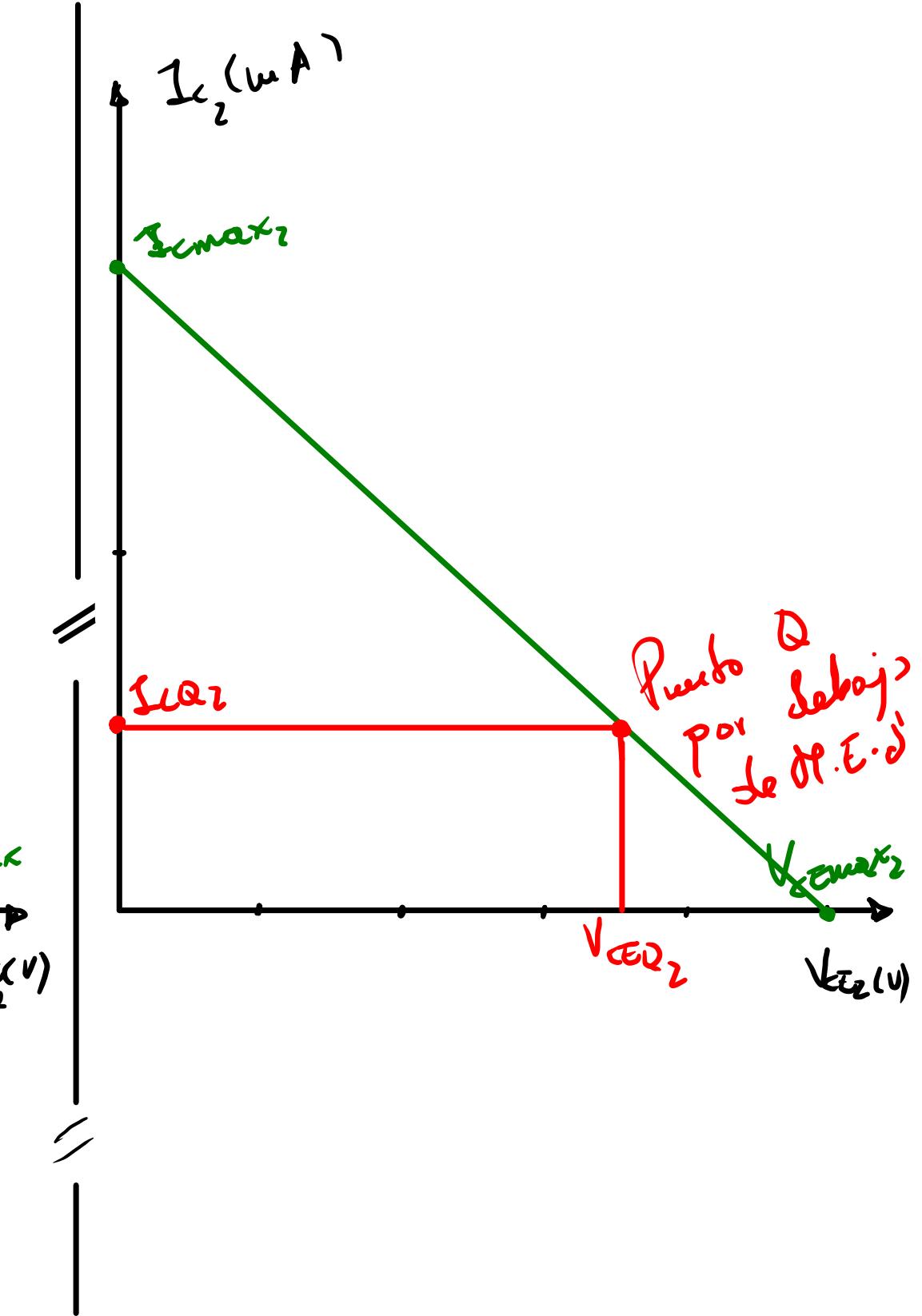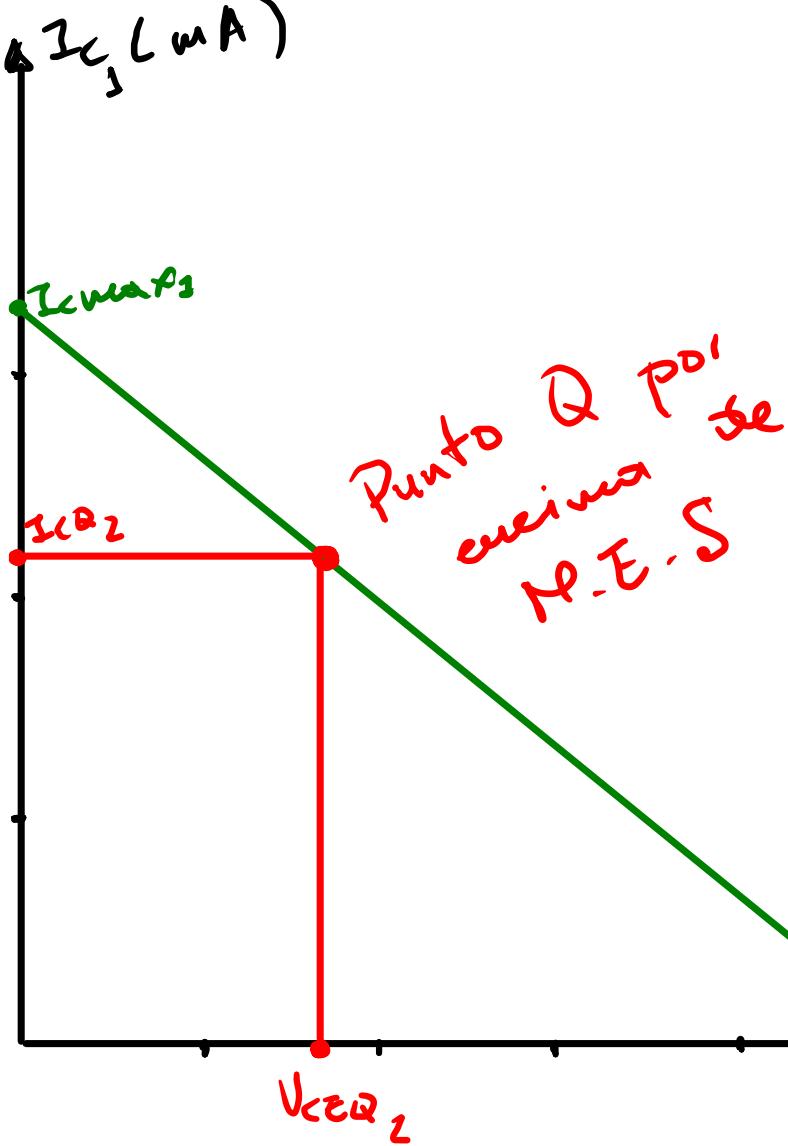

Análisis A.C

Ejercicio 2

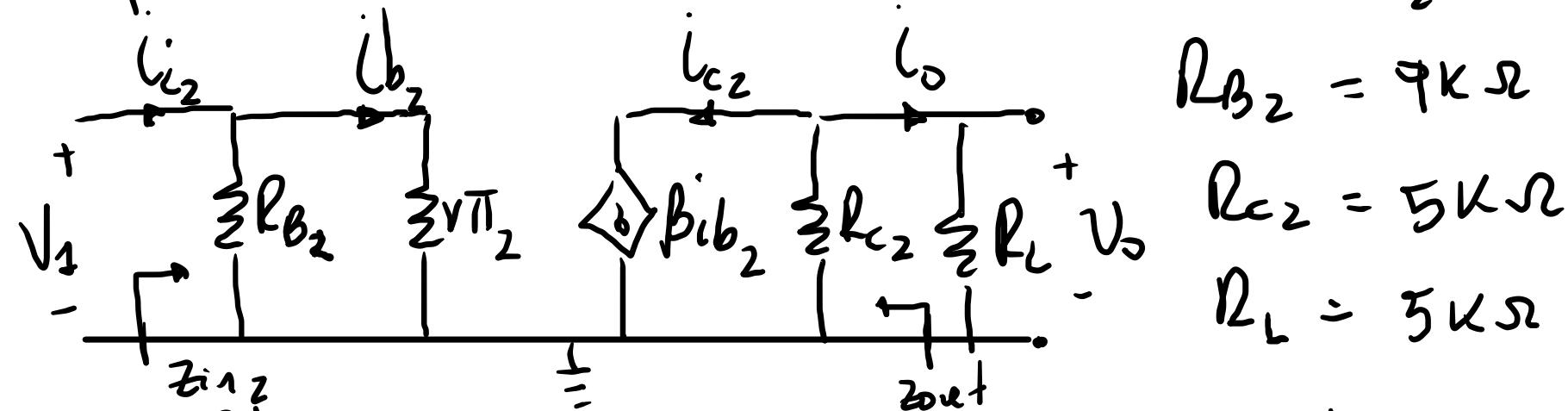

$$V\pi_2 = \frac{\beta 2G_m V}{I_{CQ2}} = 5.1 \text{ k}\Omega$$

$$R_{B2} = 9 \text{ k}\Omega$$

$$R_{C2} = 5 \text{ k}\Omega$$

$$R_L = 5 \text{ k}\Omega$$

$$A_{V2} = \frac{V_o}{V_1} \quad V_o = -\beta i_{b2} R_{C2} \| R_L ; \quad V_s = i_{b2} V\pi_2$$

$$A_{V2} = -\frac{\beta R_{C2} \| R_L i_{b2}}{i_{b2} V\pi_2} = -49.02$$

$$A_{i2} = \frac{i_o}{i_{i2}} ; \quad i_o = -\frac{\beta i_{b2} R_{C2}}{R_{C2} + R_L} ; \quad i_{b2} = \frac{i_{i2} R_{B2}}{R_{B2} + V\pi_2}$$

$$\text{Reemplazo } i_{b2} \text{ en } i_o \Rightarrow i_o = -\frac{\beta R_{C2}}{R_{C2} + R_L} \cdot \frac{i_{i2} R_{B2}}{R_{B2} + V\pi_2}$$


$$\Rightarrow \frac{i_o}{i_{i2}} = A_{i2} = -\frac{\beta R_{C2} R_{B2}}{(R_{C2} + R_L)(R_{B2} + V\pi_2)} = -32.1$$

$$Z_{in_2} = R_L' = R_{B2} \parallel r_{\pi 2} = 5.1k \parallel 9k = 3.26k\Omega$$

$$Z_{out} = R_{C2} = 5k\Omega$$

$$r_{\pi 1} = \frac{\beta 26mV}{I_{CQ1}} = 119.8\Omega$$

Etapas 1:

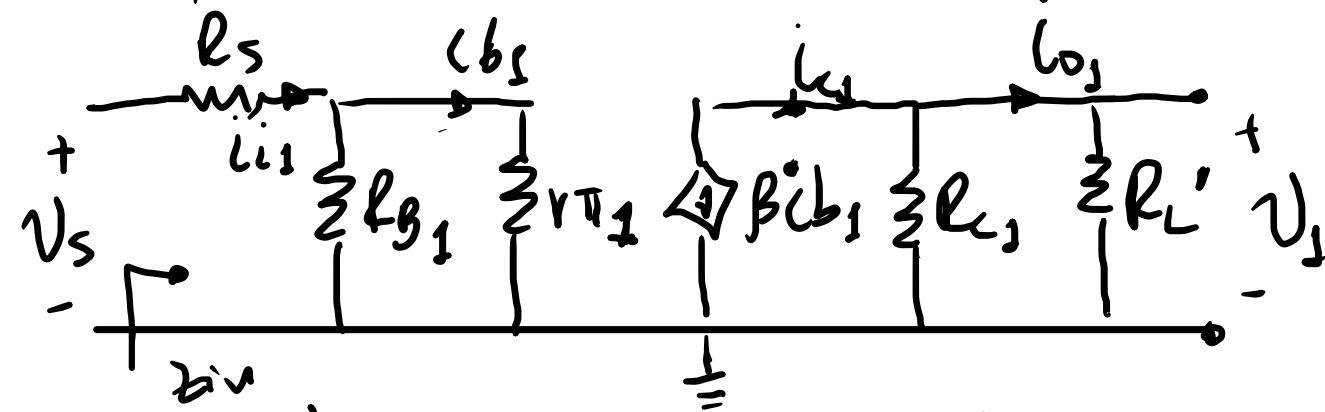

$$R_{B1} = 696.6$$

$$R_{C1} = 200$$

$$R_S = 50$$

$$R_L' = 3.26k\Omega$$

$$A_{V1} = \frac{V_1}{V_S}; \quad V_1 = -\beta i_{b1} R_{C1} \parallel R_L'; \quad V_S = i_{i1} R_S + i_{b1} r_{\pi 1}$$

$$\text{Pero } i_{b1} = \frac{i_{i1} R_{B1}}{R_{B1} + r_{\pi 1}} \Rightarrow i_{i1} = \frac{i_{b1} (R_{B1} + r_{\pi 1})}{R_{B1}}$$

$$\Rightarrow V_S = \frac{(i_{b1} (R_{B1} + r_{\pi 1})) R_S + i_{b1} r_{\pi 1}}{R_{B1}}$$

$$\Rightarrow A_{V1} = \frac{-\beta R_{C1} \parallel R_L'}{\left[\frac{(R_{B1} + r_{\pi 1}) R_S + r_{\pi 1}}{R_{B1}} \right] R_{B1}} = -105.6$$

$$A_{i_2} = \frac{i_{o_2}}{i_{i_2}} ; \quad i_{o_2} = -\frac{\beta i_{b_1} R_{C_2}}{R_{C_2} + R_i'} ; \quad i_{b_2} = \frac{i_{i_1} R_{B_1}}{R_{B_2} + r_{II_2}}$$

Reemplazando: $i_{o_2} = -\frac{\beta R_{C_2}}{R_{C_2} + R_i'} \cdot \frac{i_{i_1} R_{B_1}}{R_{B_2} + r_{II_2}}$

$$\Rightarrow \frac{i_{o_2}}{i_{i_2}} = A_{i_2} = \frac{-\beta R_{C_2} R_{B_1}}{(R_{C_2} + R_i') (R_{B_2} + r_{II_2})} = -4.93$$

$$Z_{in_1} = [R_{B_2} \parallel r_{II_2}] + R_s = 152.22 \Omega$$


$$AV_T = AV_1 * AV_2 = -49.02 * (-105.6) = 5176.5$$

$$A_{i_T} = A_{i_2} * A_{i_2} = -32.1 * (-4.93) = 158.25$$

$$Z_{in} = 152.22 \Omega$$


$$Z_{out} = 5k\Omega$$

Análisis de frecuencias bajas

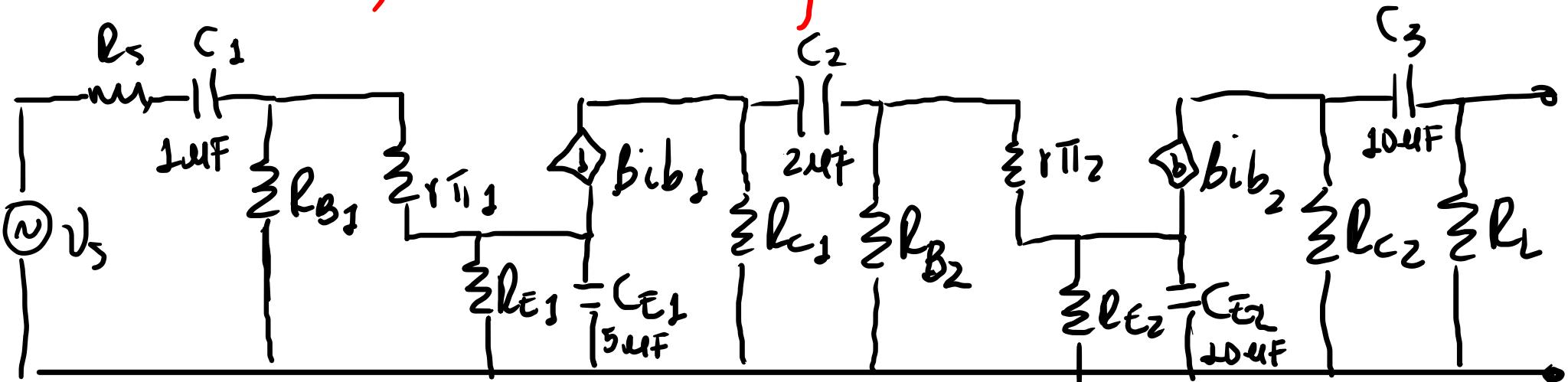

Para C_3 :

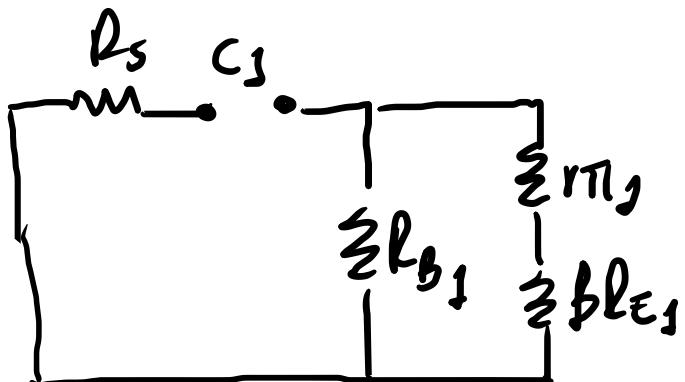- Cero en el origen
- Punto en $\omega_{p3} = \frac{1}{C_3}$; $\tilde{\tau}_3 = R_{eq3} C_3$




$$R_{eq3} = [(r_{II_3} + \beta R_{ts}) \parallel R_{B_3}] + R_s = 702 \Omega$$

$$\Rightarrow \omega_{p3} = \frac{1}{702 \times 1\mu F} = 1.42 \text{ Krad/s}$$

Para C_2 :

⇒ Cero en el origen

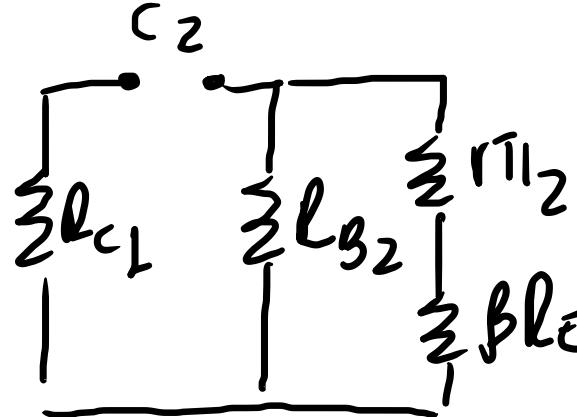⇒ Punto en $\omega_{P2} = \frac{1}{\tau_2}$; $\tau_2 = R_{eq2} C_2$




$$R_{eq2} = [(R_{c1} + \beta RL E_2) // R_{L32}] + R_{c1} = 7.94 \text{ k}\Omega$$

$$\Rightarrow \omega_{P2} = \frac{1}{7.94 \text{ k}\Omega * 2\pi F} = 62.97 \text{ rad/s}$$

Para C_3 :

⇒ Cero en el origen

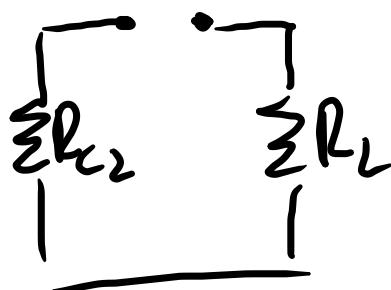⇒ Punto en $\omega_{P3} = \frac{1}{\tau_3}$; $\tau_3 = R_{eq3} C_3$




$$R_{eq3} = R_{c2} + R_L = 10 \text{ k}\Omega$$

$$\Rightarrow \omega_{P3} = \frac{1}{10 \text{ k}\Omega * 10 \text{ mF}} = 10 \text{ rad/s}$$

Para C_{E1}

$$\Rightarrow \text{Cero en } \omega_{z_1} = \frac{1}{R_{E1}C_{E1}} = \frac{1}{100 * 5\mu F} = 20 \text{ rad/s}$$
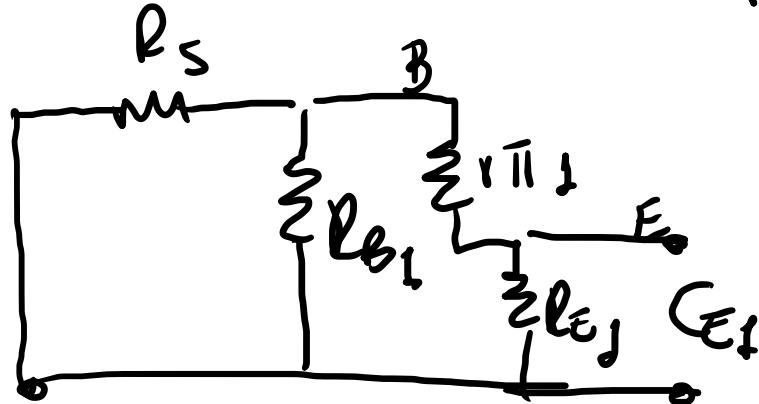
$$\Rightarrow \text{Polo en } \omega_{p_4} = \frac{1}{R_{eq4}C_{E1}}$$




$$R_{eq4} = \frac{(R_s \parallel R_{B1}) + r_{T1}}{\beta} \parallel R_{E1} = 1.64 \Omega$$

$$\Rightarrow \omega_{p_4} = \frac{1}{1.64 \Omega * 5 \mu F} = 123.9 \text{ rad/s}$$

Para C_{E2}

$$\Rightarrow \text{Cero en } \omega_{z_2} = \frac{1}{R_{E2}C_{E2}} = \frac{1}{500 * 10 \mu F} = 200 \text{ rad/s}$$
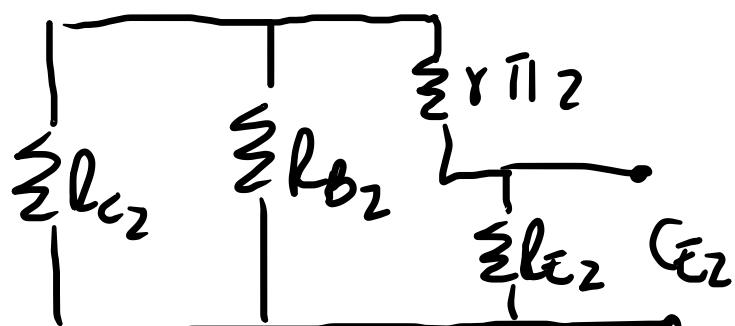
$$\Rightarrow \text{Polo en } \omega_{p_5} = \frac{1}{R_{eq5}C_{E2}}$$



$$R_{eq5} = \frac{(R_{E2} \parallel R_{B2}) + r_{T2}}{\beta} \parallel R_{E2}$$

$$R_{eq5} = 48.7$$

$$\Rightarrow \omega_{p_5} = \frac{1}{48.7 * 10 \mu F} = 20 \text{ rad/s}$$


$$\omega_{p_3} < \omega_{p_2} < \omega_{z_2} < \omega_{p_1} < \omega_{p_5} < \omega_{z_1} < \omega_{p_4}$$

10 62.97 200 1.42K 2K 2K 121K

La gráfica de la respuesta en frecuencia:

$$|A(s)|$$
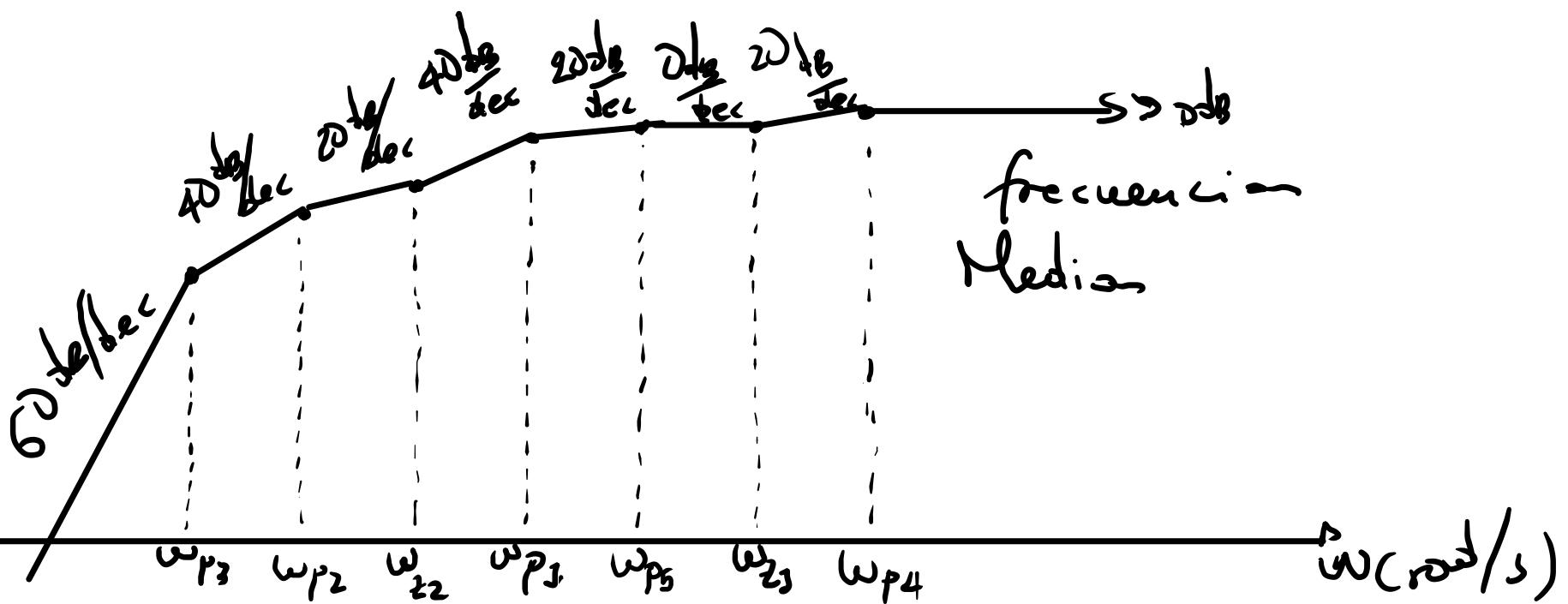
$$\omega_c = \omega_{p_4} = 121 \text{ rad/s}$$



Análisis para frecuencias altas

Hallamos C_{be_1} y C_{be_2} ; $\omega_T = 2\pi(500\text{MHz})$; $I_{CQ1} = 21.7\text{mA}$

$$C_{be_1} = \frac{g_{m1}}{\omega_T}; g_{m1} = \frac{1}{r_{e1}} = \frac{I_{CQ1}}{26\text{mV}} = 0.834 \quad C_{bc_1} = C_{bc_2} = 10\text{pF} \quad I_{CQ2} = 508.5\text{mA}$$

$$\Rightarrow C_{be_1} = \frac{0.834}{2\pi \times 500\text{MHz}} = 265.5\text{ pF}$$

$$A_{v1} = -105.6$$

$$A_{v2} = -49.02$$

$$C_{be_2} = \frac{g_{m2}}{\omega_T}; g_{m2} = \frac{1}{r_{e2}} = \frac{I_{CQ2}}{26\text{mV}} = 0.0195$$

$$C_{be_2} = \frac{0.0195}{2\pi \times 500\text{MHz}} = 6.2\text{ pF}$$

Aplicamos el teorema de Miller:

Para C_{bc_1} y C_{bc_2} :


$$CH_1 = C_{bc_1} (1 + A_{v1}) = 10\text{pF} (1 + 105.6) = 1.07\text{nF}$$

$$CH_2 = C_{bc_1} \left(1 + \frac{1}{A_{v2}} \right) = 10\text{pF} \left(1 + \frac{1}{105.6} \right) = 10.9\text{ pF}$$


$$CH_3 = C_{bc_2} (1 + A_{v2}) = 10\text{pF} (1 + 49.02) = 500.2\text{ pF}$$

$$CH_4 = C_{bc_2} \left(1 + \frac{1}{A_{v2}} \right) = 10\text{pF} \left(1 + \frac{1}{49.02} \right) = 10.2\text{ pF}$$

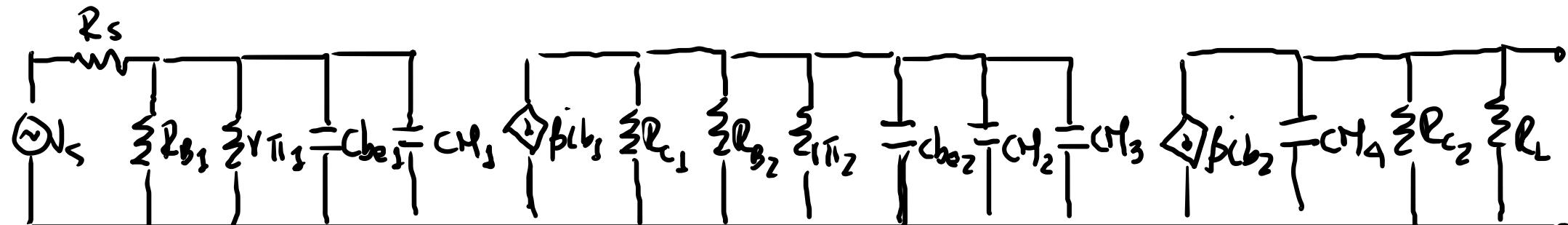El modelo equivalente para frecuencias altas queda:



Reduciendo el circuito, se obtiene:

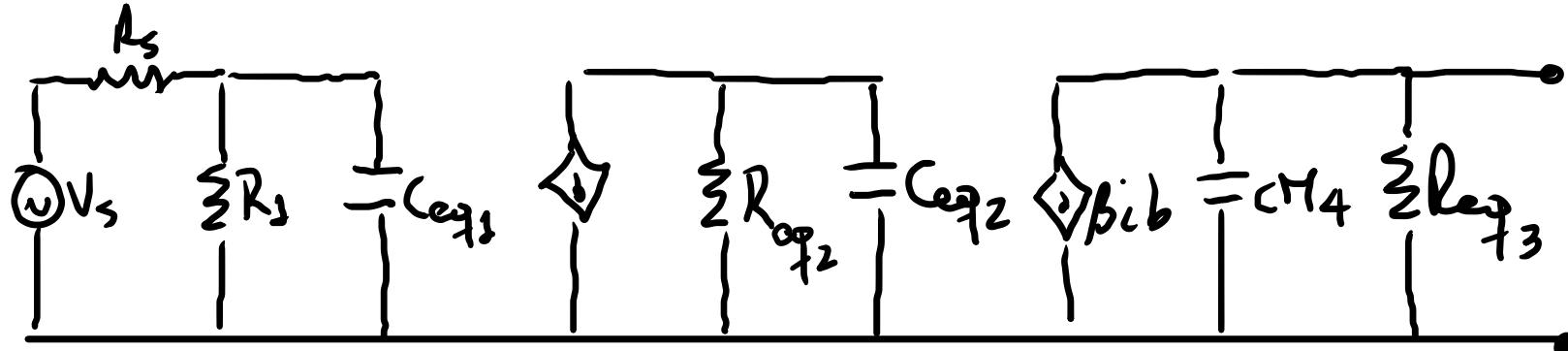

$$\text{Polo en } C_{\text{req}1}: \frac{1}{C_1} = \frac{1}{R_{\text{req}1} C_{\text{req}1}} ; \quad C_{\text{req}1} = C_{be1} + C_{M1} = \\ C_{\text{req}1} = 0.265 + 1.07 \text{ nF} = 1.335 \text{ nF}$$

$$\omega_{p1} = \frac{1}{33.57 \times 1.335 \text{ nF}} = 22.3 \text{ rad/s.}$$

$$R_{\text{req}2} = R_s \| R_1 = \left(\frac{1}{R_s} + \frac{1}{R_{B1}} + \frac{1}{r_{T1}} \right)^{-1} \\ R_{\text{req}1} = 33.57 \Omega$$

$$R_{lo} \approx C_{eq_2} \Rightarrow \omega_{p2} = \frac{1}{L_{eq_2} C_{eq_2}} ; \quad C_{eq_2} = C_{be2} + CM_2 + CM_3 = 517.3 \text{ pF}$$

6.2 pF + 10.2 pF + 500.2 pF

$$\omega_{p2} = \frac{1}{188.4 * 517.3 \text{ pF}} = 10.26 \text{ Mrad/s.} \quad R_{eq_2} = R_{C2} || R_{B2} || r_{il2}$$

$$= \left(\frac{1}{200} + \frac{1}{9k} + \frac{1}{5.8k} \right)^{-1} = 188.4 \Omega$$

para $C_{eq_3} = CM_4 = 10.2 \text{ pF}$

$$\omega_{p3} = \frac{1}{C_{eq_3} L_{eq_3}} ; \quad L_{eq_3} = R_{C2} || R_L = 2.5k\Omega$$

$$\omega_{p3} = \frac{1}{10.2 \text{ pF} * 2.5k\Omega} = 39.2 \text{ Mrad/s.}$$

En resumen $\frac{\omega_{p2}}{10.26 \text{ M}} < \frac{\omega_{p1}}{22.3 \text{ M}} < \frac{\omega_{p3}}{39.2 \text{ M}}$

$$\omega_H = \omega_{p2} = 10.26 \text{ Mrad/s}$$

La gráfica para frecuencia alta queda:

